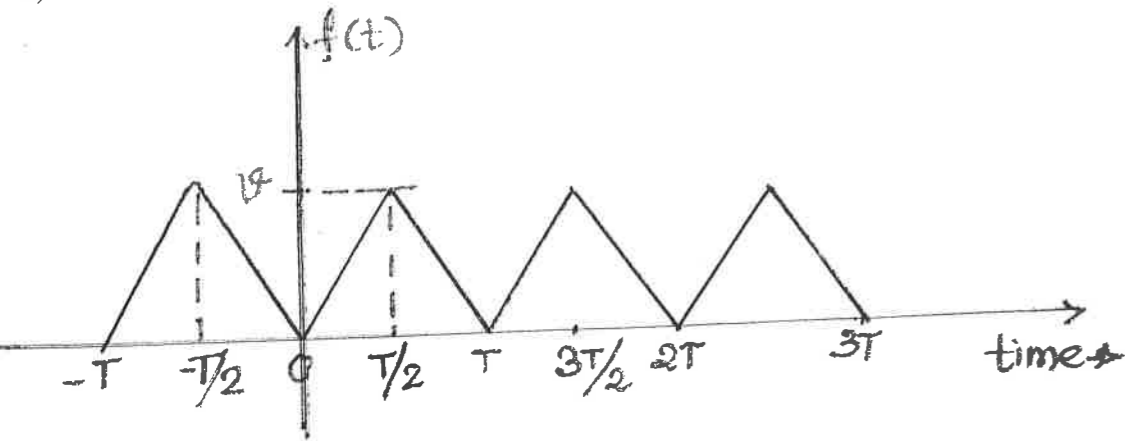



b) Derive Fourier trigonometric series for following waveform as shown below

[06]



a) For the network shown below determine transfer function  $I_1/V_2$  and  $I_2/V_1$

[06]

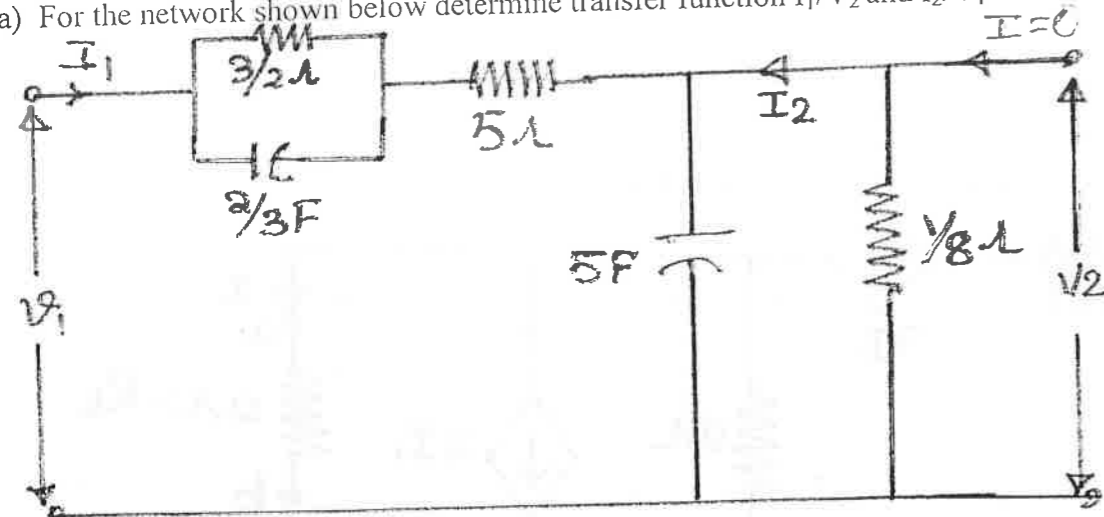

b) State maximum power transfer theorem. Derive the necessary condition for maximum power transfer by considering inductance in circuit.

Time: Three Hours


N.B:-

1. Solve any five questions.

2. Assume suitable data if necessary and state it clearly


Q.1 a) Define cut set and tie set related to graph theory, find cut set for following oriented graph as shown below. Consider 2,3,4 as tree branches.

[03]

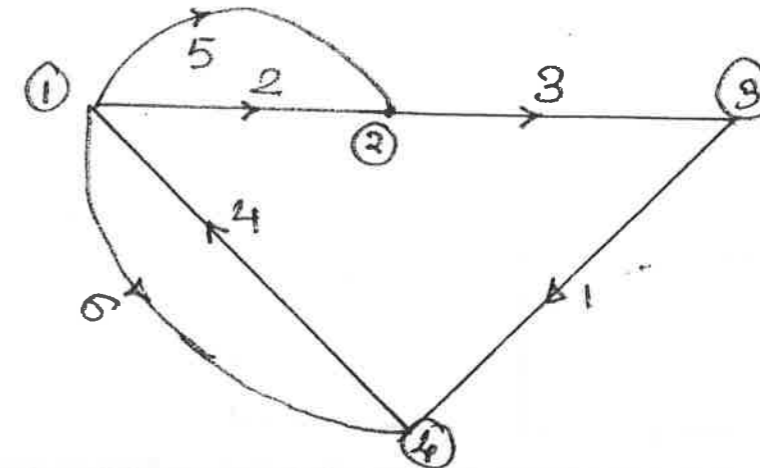

b) Find out ABCD parameter, state the circuit is reciprocal or symmetrical. Hence find out Y parameters.

[06]

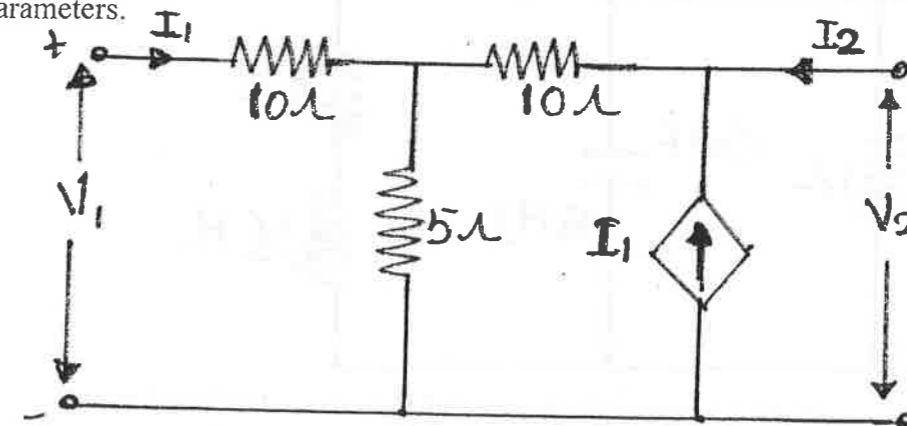


c) Starting from fundamentals, derive the Fourier transform of a unit ramp and impulse functions


[03]

Q2 a) Find voltage V across resistor on magnetically coupled circuit shown below.,

[06]

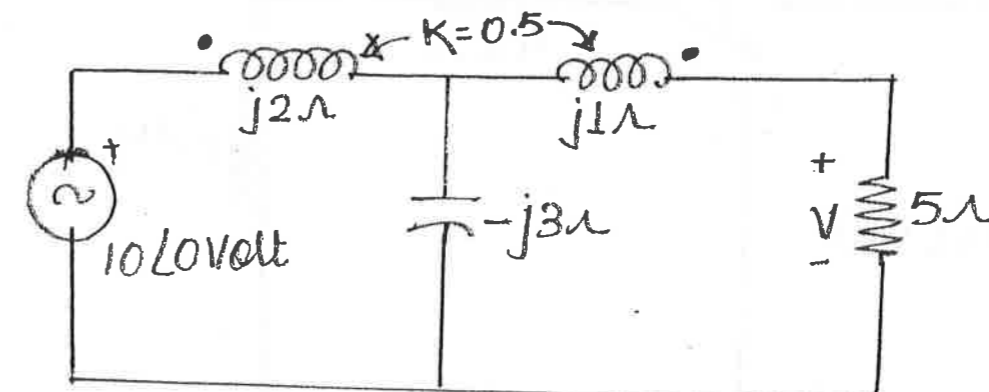


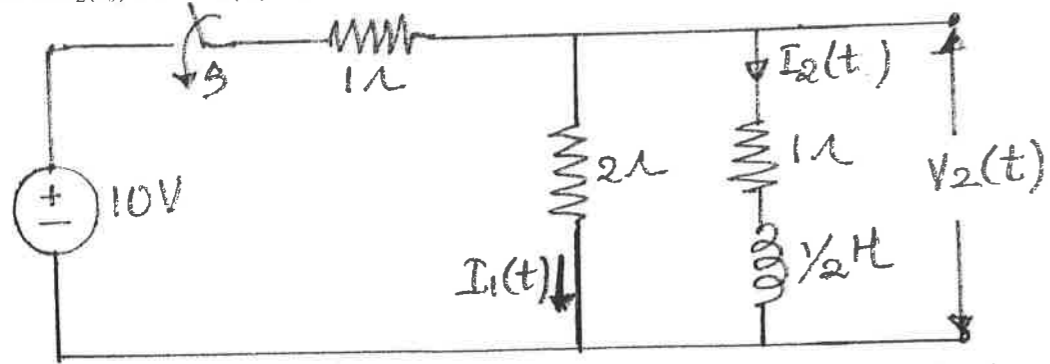- b) The circuit as shown below at time  $t_0$  after switch S was closed it is found that  $V_2 = +5$  volt. Find the value of  $I_2(t_0)$  and  $dI_2(t_0)/dt$ .




[06]

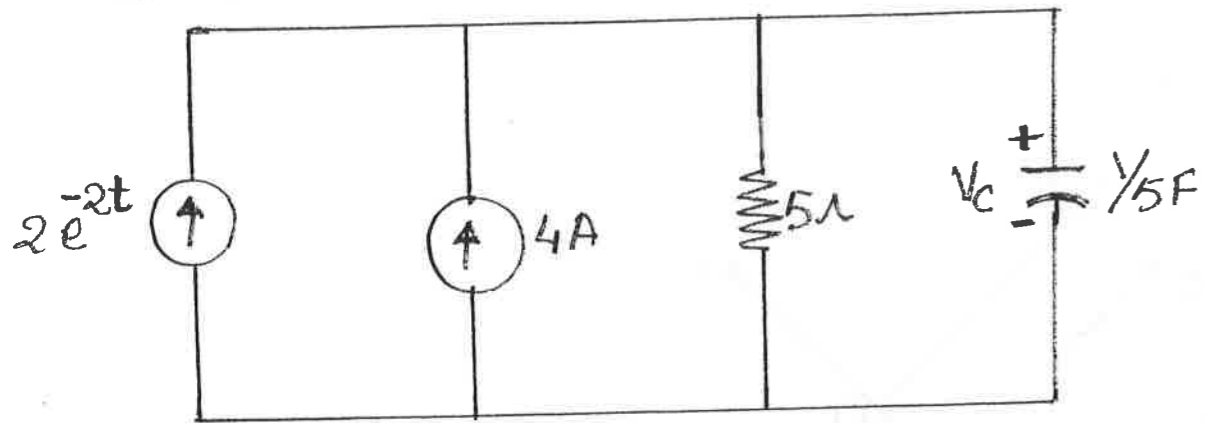- Q.3 a) In the circuit shown below initial voltage across capacitor being 5 Volt at polarity shown, find  $V_C(t)$  using time domain analysis.




[06]

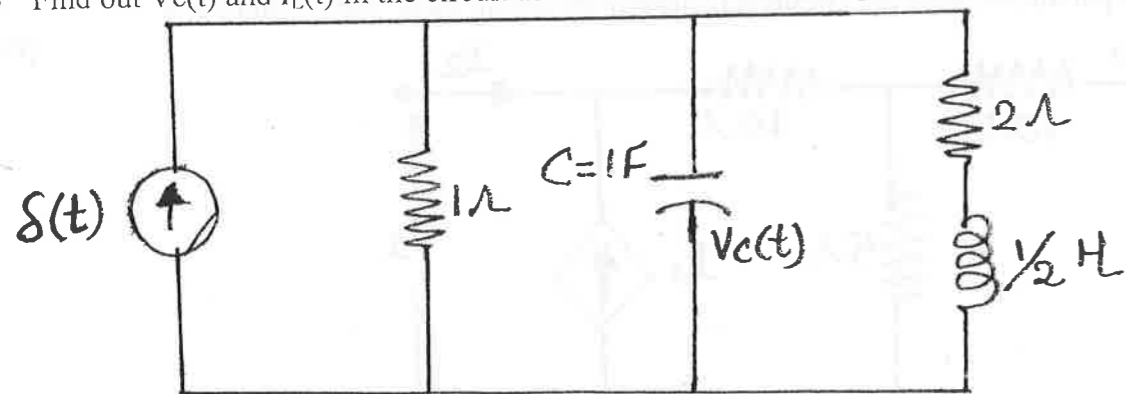- b) Find out  $V_C(t)$  and  $I_L(t)$  in the circuit as shown below. Assuming the initial condition is zero.




[06]

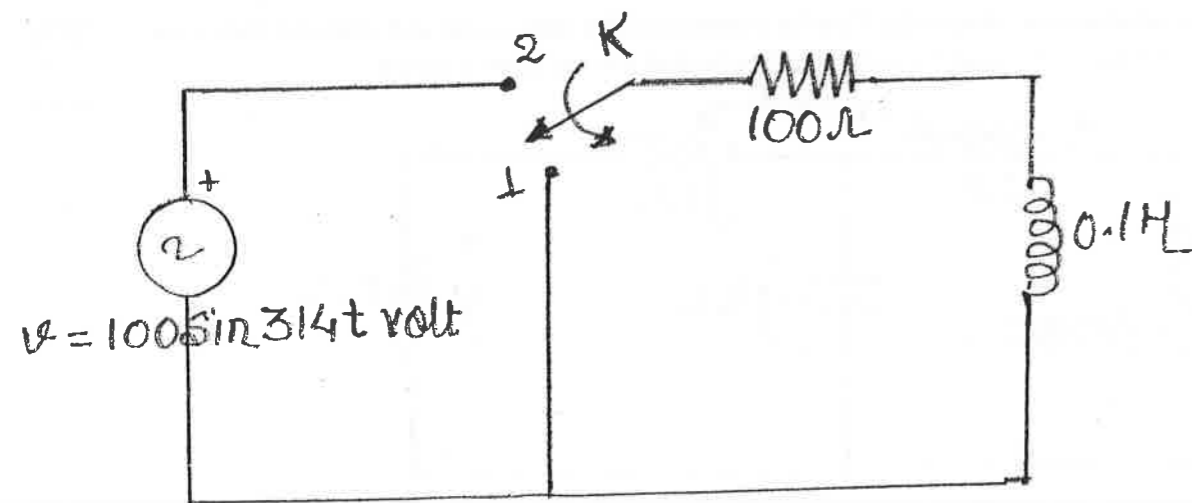- Q4 a) Obtain the current at  $t > 0$  if a. c. voltage V is applied when switch K is moved to 2 to 1 at  $t=0$ . Assume steady state current of 1Amp in LR circuits when switch was a position 1.



[06]

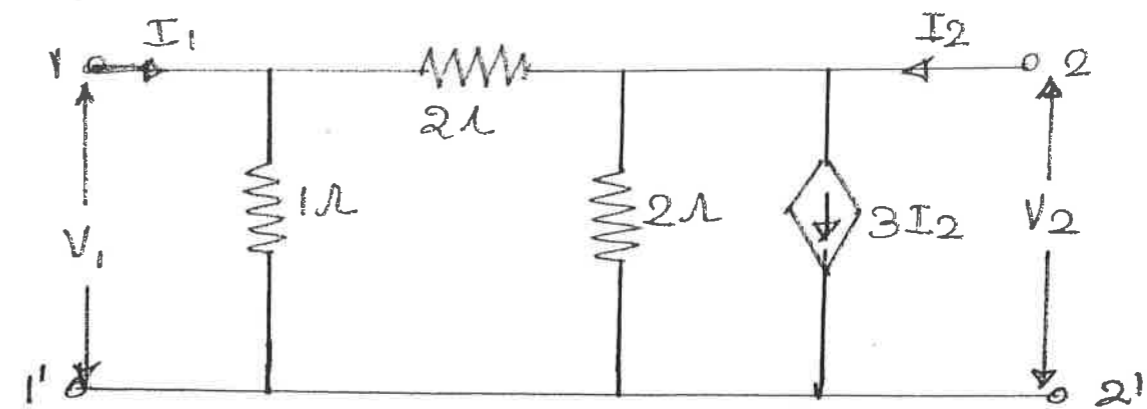- b) For the circuit shown below, find Z parameters. Hence find ABCD parameters.




[06]

- Q5 a) Define ABCD parameters. What is physical significance? Derive the condition for symmetry and reciprocity for ABCD parameters. Also find inter-relationship with H parameters.

[06]

- b) Determine current I as shown below Norton's theorem.

[06]

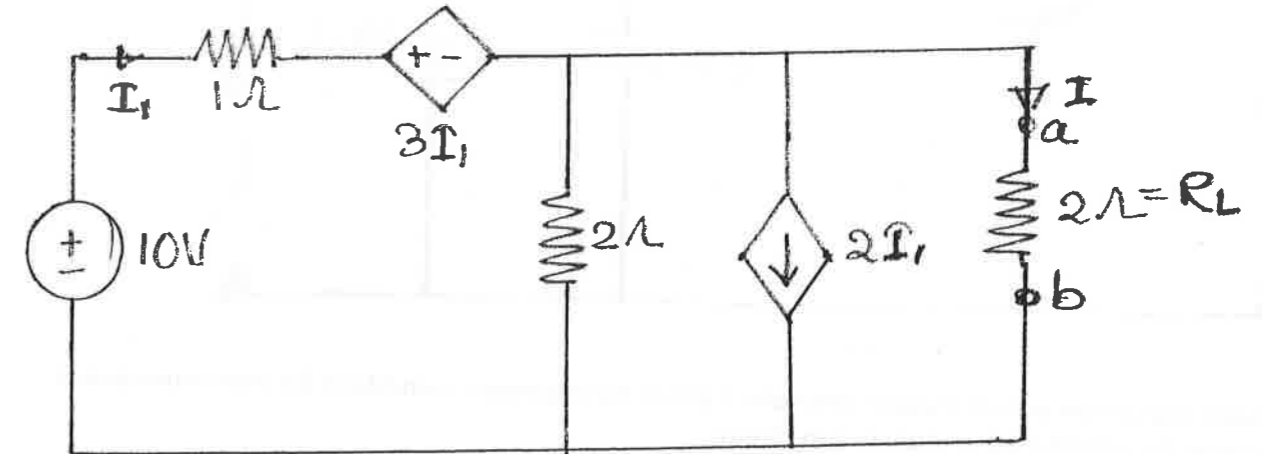

- Q.6 a) Determine  $V_1, V_2$  and  $V_3$  using super-node analysis

[06]

