

1	Q. No. 1.1	Specify the decimal equivalent of the following binary numbers expressed in the 2's complement format: (a) 00001110; (b) 10001110.
1	Q. No. 1.2	Identify the binary equivalent of (333.26) <sub>8</sub> and the octal equivalent of (1000100.0000111) <sub>2</sub>
1	Q. No. 1.3	State the binary equivalent of (17E.FF) <sub>16</sub> and the hex equivalent of (1001001110.011011100) <sub>2</sub> .
1	Q. No. 1.4	The 7's complement of a certain octal number is 5264. Determine the binary and hexadecimal equivalents of that octal number.
1	Q. No. 1.5	How many bits would be required to encode decimal numbers 0 to 9999 in straight binary and BCD codes?
1	Q. No. 1.6	Specify the excess-3 equivalent of (1111.0011) <sub>2</sub>
1	Q. No. 1.7	What would be the BCD equivalent of decimal 21 in 16-bit representation?
1	Q. No. 1.8	Find the Gray code equivalent of decimal 11
1	Q. No. 1.9	State the importance of ASCII code
1	Q. No. 1.10	Point the purpose of Hamming's Code with example
1	Q. No. 1.11	Find out whether 16-bit 2's complement arithmetic can be used to add 14 276 and 18 490
1	Q. No. 1.12	Subtract (a) (-54) <sub>10</sub> from (+31) <sub>10</sub> and Use 2's complement arithmetic.
1	Q. No. 1.13	How do you implement a four-input EX-NOR function using only two-input EX-NOR gates?
1	Q. No. 1.14	Prove AND – OR configuration is equivalent to NAND-NAND configuration
1	Q. No. 1.15	Simplify the following 1. $A B C D + A C D$ 2. $(A + 1)(A + B)$
1	Q. No. 1.16	Prove $A + \overline{A} B + A B = (A + B)$
1	Q. No. 1.17	List advantages of Analog to Digital converter
1	Q. No. 1.18	How many bits are needed to represent decimal values ranging from 0 to 10000?

- Q 3.7 Represent 2-bit comparator using Minimum Gates
- Q 3.6 Discuss in detail ALU 74181 and its applications
- Q 3.5 Represent algorithm for performing addition using subtractor

$$M(A,B,C,D) = \pi(1,2,3,5,6,7,9,11,13,14,15)$$

- Q 3.4 . Minimize the following logic function using K-map and implement it using logic gates
- Q 3.3. Design a BCD to seven segment decoder to display only " a " segment
- Q 3.2. Design a Excess -3 to BCD code converter using minimum number of NAND gates.

- a. Make a truth table for the system
- b. Write the logic expression in SOP form
- c. Realize the circuit using AND, OR gates
- d. Realize the circuit only using NAND gates

Q 3.1 A staircase light is controlled by two switches, one at the top of the stairs and another at the bottom of stairs

**Question No. 3 Attempt Any four**

Marks : 10

- Q 2.4 What are shift registers? What are different types? Illustrate PISO & PIPO registers.
- Q 2.3 Design a 3 - bit synchronous counter Use JK flip flops
- Q 2.2 Design a 4-bit asynchronous counter using a JK flip flop Explain the operation and draw the waveform.
- Q 2.1 Discuss the operation of 4-bit bidirectional shift register

**Question No. 2 Attempt any two**

Marks : 10

- Q 4.1 Explain Resolution, Linearity, accuracy, settling time and temperature sensitivity of D/A converters.
- Q 4.2 With Neat diagram explain Dual Slope A/D converter
- Q 4.3 Discuss in detail internal organization of a memory chip.
- Q 4.4 Demonstrate various Rom Configurations.
- Q 4.5 Compare & Contrast Various Memories
- Q 4.6 Illustrate with necessary diagram working of R/ZR digital to analog converter

**Question No. 4 Attempt any three(03)**

CO3

Marks : 12

**Question 5**

CO4

Marks : 16

- Q 5.1 Explain General Moore machine model and compare with Mealy machine model with necessary diagram.
- Q 5.2 Illustrate in detail sequential machine synthesis procedure
- Q 5.3 Design a sequential circuit using T flip flop for the state diagram shown below.

